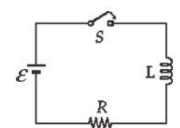


ANSWERS

<p>1</p>	<p>From $\mathcal{E} = L \left(\frac{\Delta i}{\Delta t} \right)$, we have</p> $L = \frac{ \mathcal{E} }{ \Delta i / \Delta t } = \frac{ \mathcal{E} (\Delta t)}{ \Delta i } = \frac{(12.0 \times 10^{-3} \text{ V})(0.500 \text{ s})}{ 2.00 \text{ A} - 3.50 \text{ A} }$ $= 4.00 \times 10^{-3} \text{ H} = \boxed{4.00 \text{ mH}}$ <p style="text-align: right;">Note: Given values in this assignment may vary.</p>
<p>2</p>	<p>The inductance is $L = \frac{\mu_0 N^2 A}{\ell}$ with $A = \pi r^2$. The induced emf as a function of time is $\mathcal{E}_L = -L \frac{di}{dt}$. By substitution we have</p> $\mathcal{E}_L = -L \frac{di}{dt} = -\frac{\mu_0 N^2 \pi r^2}{\ell} \frac{di}{dt} \quad \text{and} \quad r = \left(\frac{-\mathcal{E}_L \ell}{\mu_0 N^2 \pi di/dt} \right)^{1/2}$ <p>Then</p> $r = \left(\frac{-(175 \times 10^{-6} \text{ V})(0.160 \text{ m})}{(4\pi \times 10^{-7} \text{ N/A}^2)(420)^2 \pi (-0.421 \text{ A/s})} \right)^{1/2} = \boxed{9.77 \text{ mm}}$
<p>3</p>	<p>(a) The inductance of a solenoid is</p> $L = \frac{\mu_0 N^2 A}{\ell} = \frac{\mu_0 N^2 \pi r^2}{\ell} = \frac{\mu_0 (510)^2 \pi (8.00 \times 10^{-3} \text{ m})^2}{0.140 \text{ m}}$ $= 4.69 \times 10^{-4} \text{ H} = \boxed{0.469 \text{ mH}}$ <p>(b) The time constant of the circuit is</p> $\tau = \frac{L}{R} = \frac{4.69 \times 10^{-4} \text{ H}}{2.50 \Omega} = 1.88 \times 10^{-4} \text{ s} = \boxed{0.188 \text{ ms}}$
<p>4</p>	<p>At time t:</p> $i(t) = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) \quad \text{where} \quad \tau = \frac{2.7}{20} = 0.135$ <p>After a long time,</p> $i = \frac{\mathcal{E}}{R} (1 - e^{-\infty}) = \frac{\mathcal{E}}{R}$ <p>a) Current reach 50% of its final value: $i(t) = \frac{50}{100} i$,</p> <p>Thus $\frac{i(t)}{i} = 0.5$:</p> $\frac{i(t)}{i} = \frac{\mathcal{E}/R (1 - e^{-t/\tau})}{\mathcal{E}/R} = (1 - e^{-t/\tau})$ <p>Solve $0.5 = (1 - e^{-\frac{t}{0.135}})$, note: $\tau = \frac{2.7}{20} = 0.135$</p> $e^{-\frac{t}{0.135}} = 1 - 0.5 = 0.5 \rightarrow \ln(0.5) = -\frac{t}{0.135} \rightarrow 0.69 = \frac{t}{0.135} \rightarrow \boxed{t = 0.09 \text{ (s)}}$ <p>b) Current reach 90% of its final value: $i(t) = \frac{90}{100} i$,</p> <p>Thus $\frac{i(t)}{i} = 0.9$</p> <p>Similarly solve $0.9 = (1 - e^{-\frac{t}{0.135}})$</p> $e^{-\frac{t}{0.135}} = 1 - 0.9 = 0.1 \rightarrow \ln(0.1) = -\frac{t}{0.135} \rightarrow 2.3 = \frac{t}{0.135} \rightarrow \boxed{t = 0.31 \text{ (s)}}$ <p>(c) We require $i = 0.500 i_f = \frac{0.500 \mathcal{E}}{R}$, or</p> $0.500 \frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R} e^{-t/\tau} \rightarrow e^{-t/\tau} = 0.500$ <p>taking natural logarithm of both sides,</p> $\ln(e^{-t/\tau}) = \ln(0.500) \rightarrow -\frac{t}{\tau} = -\ln(2.00)$ <p>where we have used the identity $\ln\left(\frac{1}{x}\right) = -\ln(x)$. Solving for the time t gives</p> $t = \tau(\ln(2.00)) = \frac{L}{R}(\ln(2.00)) = \frac{2.30 \text{ H}}{16.0 \Omega}(\ln(2.00)) = 0.0996 \text{ s}$ <p>(d) In this case, $i = 0.100 i_f = \frac{0.100 \mathcal{E}}{R}$, or</p> $0.100 \frac{\mathcal{E}}{R} = \frac{\mathcal{E}}{R} e^{-t/\tau} \rightarrow e^{-t/\tau} = 0.100$ <p>taking natural logarithm of both sides,</p> $\ln(e^{-t/\tau}) = \ln(0.100) \rightarrow -\frac{t}{\tau} = -\ln(10.0)$ <p>where we have used the identity $\ln\left(\frac{1}{x}\right) = -\ln(x)$. Solving for the time t gives</p> $t = \tau(\ln(10.0)) = \frac{L}{R}(\ln(10.0)) = \frac{2.30 \text{ H}}{16.0 \Omega}(\ln(10.0)) = 0.331 \text{ s}$
<p>5</p>	<div style="display: flex; align-items: center;"> <div style="flex: 1;"> <p>(a) $\tau = \frac{L}{R} = \frac{8.00 \times 10^{-3} \text{ H}}{4.00 \Omega} = 2.00 \times 10^{-3} \text{ s} = \boxed{2.00 \text{ ms}}$</p> <p>(b) $i = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau}) = \left(\frac{6.00 \text{ V}}{4.00 \Omega} \right) (1 - e^{-0.250/2.00}) = \boxed{0.176 \text{ A}}$</p> <p>(c) $I_i = \frac{\mathcal{E}}{R} = \frac{6.00 \text{ V}}{4.00 \Omega} = \boxed{1.50 \text{ A}}$</p> <p>(d) $0.800 = 1 - e^{-t/2.00 \text{ ms}} \rightarrow t = -(2.00 \text{ ms}) \ln(0.200) = \boxed{3.22 \text{ ms}}$</p> </div> <div style="flex: 0.5; text-align: center;">  </div> </div>

6	<p>For a solenoid of length ℓ, the inductance is $L = \frac{\mu_0 N^2 A}{\ell}$.</p> <p>Thus, since $U_B = \frac{1}{2} Li^2 = \frac{\mu_0 N^2 A i^2}{2\ell}$, the stored energy is</p> $U_B = \frac{(4\pi \times 10^{-7} \text{ N/A}^2)(68)^2 \pi (6.00 \times 10^{-3} \text{ m})^2 (0.770 \text{ A})^2}{2 (0.0800 \text{ m})}$ $= \boxed{2.44 \times 10^{-6} \text{ J}}$
7	<p>(a) The magnetic energy density is given by</p> $u_B = \frac{B^2}{2\mu_0} = \frac{(4.50 \text{ T})^2}{2(4\pi \times 10^{-7} \text{ T} \cdot \text{m/A})} = 8.06 \times 10^6 \text{ J/m}^3 = \boxed{8.06 \text{ MJ}}$ <p>(b) The magnetic energy stored in the field equals u times the volume of the solenoid (the volume in which B is non-zero).</p> $U_B = u_B V = (8.06 \times 10^6 \text{ J/m}^3) [(0.260 \text{ m})\pi(0.0310 \text{ m})^2]$ $= \boxed{6.32 \text{ kJ}}$
8	<p>This radio is a radiotelephone on a ship, according to frequency assignments made by international treaties, laws, and decisions of the National Telecommunications and Information Administration.</p> <p>The resonance frequency is $f_0 = \frac{1}{2\pi\sqrt{LC}}$.</p> <p>Thus, $C = \frac{1}{(2\pi f_0)^2 L} = \frac{1}{[2\pi(6.30 \times 10^6 \text{ Hz})]^2 (1.05 \times 10^{-6} \text{ H})} = \boxed{608 \text{ pF}}$</p>
9	<p>(a) The frequency of oscillation of the circuit is</p> $f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(0.100 \text{ H})(1.00 \times 10^{-6} \text{ F})}} = \boxed{503 \text{ Hz}}$ <p>(b) The maximum charge on the capacitor is</p> $Q = C\mathcal{E} = (1.00 \times 10^{-6} \text{ F})(12.0 \text{ V}) = \boxed{12.0 \mu\text{C}}$ <p>(c) To find the maximum current I_i, we equate</p> $\frac{1}{2} C\mathcal{E}^2 = \frac{1}{2} LI_i^2$ <p>Then solve for I_i to obtain</p> $I_i = \mathcal{E} \sqrt{\frac{C}{L}} = 12.0 \text{ V} \sqrt{\frac{1.00 \times 10^{-6} \text{ F}}{0.100 \text{ H}}} = \boxed{37.9 \text{ mA}}$ <p>(d) The total energy the circuit possesses at $t = 3.00 \text{ s}$ and at all times is</p> $U = \frac{1}{2} C\mathcal{E}^2 = \frac{1}{2} (1.00 \times 10^{-6} \text{ F})(12.0 \text{ V})^2 = \boxed{72.0 \mu\text{J}}$