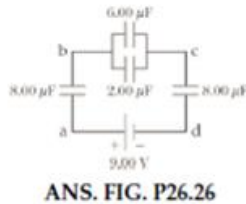


Prb. #	ANSWERS	
1	<p>(a) <math>Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(12.0 \text{ V}) = 4.80 \times 10^{-5} \text{ C} = \boxed{48.0 \mu\text{C}}</math></p> <p>(b) <math>Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(1.50 \text{ V}) = 6.00 \times 10^{-6} \text{ C} = \boxed{6.00 \mu\text{C}}</math></p>	<p>Note: Throughout this assignment, the given values of certain parameters, such as C and V, may vary</p>
2	<p>(a) <math>C = \frac{\kappa \epsilon_0 A}{d} = \frac{(1.00)(8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2)(2.30 \times 10^{-4} \text{ m}^2)}{1.50 \times 10^{-3} \text{ m}} = 1.36 \times 10^{-12} \text{ F} = \boxed{1.36 \text{ pF}}</math></p> <p>(b) <math>Q = C\Delta V = (1.36 \text{ pF})(12.0 \text{ V}) = \boxed{16.3 \text{ pC}}</math></p> <p>(c) <math>E = \frac{\Delta V}{d} = \frac{12.0 \text{ V}}{1.50 \times 10^{-3} \text{ m}} = \boxed{8.00 \times 10^3 \text{ V/m}}</math></p>	
3	<p>(a) For a spherical capacitor with inner radius <math>a</math> and outer radius <math>b</math>,</p> $C = \frac{4\pi\epsilon_0 ab}{k_e(b-a)} = \frac{(8.85 \times 10^{-12} \text{ F/m})(0.0700 \text{ m})(0.140 \text{ m})}{(8.99 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2)(0.140 \text{ m} - 0.0700 \text{ m})} = \boxed{15.6 \text{ pF}}$ <p>(b) <math>\Delta V = \frac{Q}{C} = \frac{4.00 \times 10^{-6} \text{ C}}{1.56 \times 10^{-11} \text{ F}} = 2.57 \times 10^5 \text{ V} = \boxed{257 \text{ kV}}</math></p>	<p>(c) Solution to <b>What If?</b></p> <p>Set the capacitance of a cylindrical capacitor, given by <math>C = \frac{2\pi\epsilon_0 \ell}{k_e \ln(b/a)}</math>, equal to that of a spherical capacitor, given by <math>C = \frac{4\pi\epsilon_0 ab}{k_e(b-a)}</math>, and solve for the length of the cylindrical capacitor.</p> $C_{\text{cylinder}} = C_{\text{sphere}} \rightarrow \frac{2\pi\epsilon_0 \ell}{k_e \ln(b/a)} = \frac{4\pi\epsilon_0 ab}{k_e(b-a)} \rightarrow \ell = \frac{2ab}{(b-a)} \ln\left(\frac{b}{a}\right)$ <p>Substituting numerical values,</p> $\ell = \frac{2(6.70 \text{ cm})(15.0 \text{ cm})}{(15.0 \text{ cm} - 6.70 \text{ cm})} \ln\left(\frac{15.0 \text{ cm}}{6.70 \text{ cm}}\right) = 19.5 \text{ cm}$
4	<p>(a) When connected in series, the equivalent capacitance is</p> $\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}, \text{ or}$ $\frac{1}{C_{\text{eq}}} = \frac{1}{4.20 \mu\text{F}} + \frac{1}{8.50 \mu\text{F}} \rightarrow C_{\text{eq}} = \boxed{2.81 \mu\text{F}}$ <p>(b) When connected in parallel, the equivalent capacitance is</p> $C_{\text{eq}} = C_1 + C_2 = 4.20 \mu\text{F} + 8.50 \mu\text{F} = \boxed{12.70 \mu\text{F}}$	
5	<p>(a) <math>C = \frac{\kappa \epsilon_0 A}{d} = \frac{2.10(8.85 \times 10^{-12} \text{ F/m})(1.75 \times 10^{-4} \text{ m}^2)}{4.00 \times 10^{-5} \text{ m}} = 8.13 \times 10^{-11} \text{ F} = \boxed{81.3 \text{ pF}}</math></p> <p>(b) <math>\Delta V_{\text{max}} = E_{\text{max}}d = (60.0 \times 10^6 \text{ V/m})(4.00 \times 10^{-5} \text{ m}) = \boxed{2.40 \text{ kV}}</math></p>	
6	<p>(a) First, we replace the parallel combination between points b and c by its equivalent capacitance, <math>C_{bc} = 2.00 \mu\text{F} + 6.00 \mu\text{F} = 8.00 \mu\text{F}</math>. Then, we have three capacitors in series between points a and d. The equivalent capacitance for this circuit is therefore</p> $\frac{1}{C_{\text{eq}}} = \frac{1}{C_{ab}} + \frac{1}{C_{bc}} + \frac{1}{C_{cd}} = \frac{3}{8.00 \mu\text{F}}$ <p>giving</p> $C_{\text{eq}} = \frac{8.00 \mu\text{F}}{3} = \boxed{2.67 \mu\text{F}}$ <p>(b) The charge on each capacitor in the series is the same as the charge on the equivalent capacitor:</p> $Q_{ab} = Q_{bc} = Q_{cd} = C_{\text{eq}}(\Delta V_{ad}) = (2.67 \mu\text{F})(9.00 \text{ V}) = 24.0 \mu\text{C}$	<p>Then, note that <math>\Delta V_{bc} = \frac{Q_{bc}}{C_{bc}} = \frac{24.0 \mu\text{C}}{8.00 \mu\text{F}} = 3.00 \text{ V}</math>. The charge on each capacitor in the original circuit is:</p> <p>On the <math>8.00 \mu\text{F}</math> between a and b:</p> $Q_5 = Q_{ab} = \boxed{24.0 \mu\text{C}}$ <p>On the <math>8.00 \mu\text{F}</math> between c and d:</p> $Q_6 = Q_{cd} = \boxed{24.0 \mu\text{C}}$ <p>On the <math>2.00 \mu\text{F}</math> between b and c:</p> $Q_2 = C_2(\Delta V_{bc}) = (2.00 \mu\text{F})(3.00 \text{ V}) = \boxed{6.00 \mu\text{C}}$ <p>On the <math>6.00 \mu\text{F}</math> between b and c:</p> $Q_6 = C_6(\Delta V_{bc}) = (6.00 \mu\text{F})(3.00 \text{ V}) = \boxed{18.0 \mu\text{C}}$ <p>(c) We earlier found that <math>\Delta V_{bc} = 3.00 \text{ V}</math>. The two <math>8.00 \mu\text{F}</math> capacitors have the same voltage: <math>\Delta V_5 = \Delta V_6 = \frac{Q}{C} = \frac{24.0 \mu\text{C}}{8.00 \mu\text{F}} = 3.00 \text{ V}</math>, so we conclude that the potential difference across each capacitor is the same: <math>\Delta V_5 = \Delta V_2 = \Delta V_6 = \Delta V_3 = \boxed{3.00 \text{ V}}</math>.</p>



7

- (a) We simplify the circuit of Figure P26.23 in three steps as shown in ANS. FIG. P26.23 panels (a), (b), and (c). First, the  $15.0\text{-}\mu\text{F}$  and  $3.00\text{-}\mu\text{F}$  capacitors in series are equivalent to




$$\frac{1}{(1/15.0\ \mu\text{F}) + (1/3.00\ \mu\text{F})} = 2.50\ \mu\text{F}$$

Next, the  $2.50\text{-}\mu\text{F}$  capacitor combines in parallel with the  $6.00\text{-}\mu\text{F}$  capacitor, creating an equivalent capacitance of  $8.50\ \mu\text{F}$ . At last, this  $8.50\text{-}\mu\text{F}$  equivalent capacitor and the  $20.0\text{-}\mu\text{F}$  capacitor are in series, equivalent to

$$\frac{1}{(1/8.50\ \mu\text{F}) + (1/20.00\ \mu\text{F})} = \boxed{5.96\ \mu\text{F}}$$

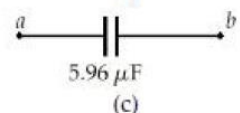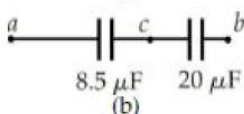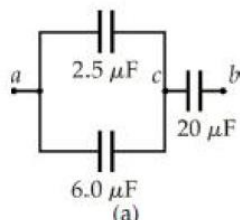- (b) We find the charge on each capacitor and the voltage across each by working backwards through solution figures (c)–(a), alternately applying  $Q = C\Delta V$  and  $\Delta V = Q/C$  to every capacitor, real or equivalent. For the  $5.96\text{-}\mu\text{F}$  capacitor, we have

$$Q = C\Delta V = (5.96\ \mu\text{F})(15.0\ \text{V}) = \boxed{89.5\ \mu\text{C}}$$



ANS. FIG. P26.23

Thus, if  $a$  is higher in potential than  $b$ , just  $89.5\ \mu\text{C}$  flows between the wires and the plates to charge the capacitors in each picture. In (b) we have, for the  $8.5\text{-}\mu\text{F}$  capacitor,

$$\Delta V_{ac} = \frac{Q}{C} = \frac{89.5\ \mu\text{C}}{8.50\ \mu\text{F}} = 10.5\ \text{V}$$

and for the  $20.0\text{-}\mu\text{F}$  capacitor in (b), (a), and the original circuit, we have  $Q_{20} = 89.5\ \mu\text{C}$ . Then

$$\Delta V_{cb} = \frac{Q}{C} = \frac{89.5\ \mu\text{C}}{20.0\ \mu\text{F}} = 4.47\ \text{V}$$

Next, the circuit in diagram (a) is equivalent to that in (b), so  $\Delta V_{cb} = 4.47\ \text{V}$  and  $\Delta V_{ac} = 10.5\ \text{V}$ .

For the  $2.50\text{-}\mu\text{F}$  capacitor,  $\Delta V = 10.5\ \text{V}$  and

$$Q = C\Delta V = (2.50\ \mu\text{F})(10.5\ \text{V}) = \boxed{26.3\ \mu\text{C}}$$

For the  $6.00\text{-}\mu\text{F}$  capacitor,  $\Delta V = 10.5\ \text{V}$  and

$$Q_6 = C\Delta V = (6.00\ \mu\text{F})(10.5\ \text{V}) = \boxed{63.2\ \mu\text{C}}$$

Now,  $26.3\ \mu\text{C}$  having flowed in the upper parallel branch in (a), back in the original circuit we have  $Q_{15} = 26.3\ \mu\text{C}$  and  $Q_3 = 26.3\ \mu\text{C}$ .

8

(a)  $U_E = \frac{1}{2}C(\Delta V)^2 = \frac{1}{2}(3.00\ \mu\text{F})(12.0\ \text{V})^2 = \boxed{216\ \text{J}}$

(b)  $U_E = \frac{1}{2}C(\Delta V)^2 = \frac{1}{2}(3.00\ \mu\text{F})(6.00\ \text{V})^2 = \boxed{54.0\ \text{J}}$

9

From  $U_E = \frac{1}{2}C\Delta V^2$ , we have

$$U_E = \frac{1}{2}(31.8 \times 10^{-6}\ \text{F})(4.35 \times 10^3\ \text{V})^2 = 301\ \text{J}$$

10

- (a) The equivalent capacitance of a series combination of  $C_1$  and  $C_2$  is

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{18.0\ \mu\text{F}} + \frac{1}{36.0\ \mu\text{F}} \rightarrow C_{\text{eq}} = \boxed{12.0\ \mu\text{F}}$$

- (b) This series combination is connected to a  $12.0\text{-V}$  battery, the total stored energy is

$$U_{E,\text{eq}} = \frac{1}{2}C_{\text{eq}}(\Delta V)^2 = \frac{1}{2}(12.0 \times 10^{-6}\ \text{F})(12.0\ \text{V})^2 = \boxed{8.64 \times 10^{-4}\ \text{J}}$$

- (c) Capacitors in series carry the same charge as their equivalent capacitor. The charge stored on each of the two capacitors in the series combination is

$$Q_1 = Q_2 = Q_{\text{total}} = C_{\text{eq}}(\Delta V) = (12.0\ \mu\text{F})(12.0\ \text{V}) = 144\ \mu\text{C} = 1.44 \times 10^{-4}\ \text{C}$$

and the energy stored in each of the individual capacitors is:

$18.0\ \mu\text{F}$  capacitor:

$$U_{E1} = \frac{Q_1^2}{2C_1} = \frac{(1.44 \times 10^{-4}\ \text{C})^2}{2(18.0 \times 10^{-6}\ \text{F})} = \boxed{5.76 \times 10^{-4}\ \text{J}}$$

$36.0\ \mu\text{F}$  capacitor:

$$U_{E2} = \frac{Q_2^2}{2C_2} = \frac{(1.44 \times 10^{-4}\ \text{C})^2}{2(36.0 \times 10^{-6}\ \text{F})} = \boxed{2.88 \times 10^{-4}\ \text{J}}$$

- (d)  $U_{E1} + U_{E2} = 5.76 \times 10^{-4}\ \text{J} + 2.88 \times 10^{-4}\ \text{J} = 8.64 \times 10^{-4}\ \text{J} = U_{E,\text{eq}}$ , which is one reason why the  $12.0\ \mu\text{F}$  capacitor is considered to be equivalent to the two capacitors.

- (e) The total energy of the equivalent capacitance will always equal the sum of the energies stored in the individual capacitors.

- (f) If  $C_1$  and  $C_2$  were connected in parallel rather than in series, the equivalent capacitance would be  $C_{\text{eq}} = C_1 + C_2 = 18.0\ \mu\text{F} + 36.0\ \mu\text{F} = 54.0\ \mu\text{F}$ . If the total energy stored in this parallel combination is to be the same as stored in the original series combination, it is necessary that

$$\frac{1}{2}C_{\text{eq}}(\Delta V)^2 = U_{E,\text{eq}}$$

From which we obtain

$$\Delta V = \sqrt{\frac{2U_{E,\text{eq}}}{C_{\text{eq}}}} = \sqrt{\frac{2(8.64 \times 10^{-4}\ \text{J})}{54.0 \times 10^{-6}\ \text{F}}} = \boxed{5.66\ \text{V}}$$

- (g) Because the potential difference is the same across the two capacitors when connected in parallel, and  $U_E = \frac{1}{2}C(\Delta V)^2$ , the larger capacitor  $C_2$  stores more energy.